

# Project 1 - Hardware Basics

Todd Hayes, Martin Heberling, Justin Hu, Manley Roberts, Colin Sergi, Jordan Ogrinc

Fall 2020

## Contents

<b>1</b>	<b>Introduction</b>	<b>3</b>
<b>2</b>	<b>Setup</b>	<b>3</b>
<b>3</b>	<b>Part 1 — Introduction to CircuitSim</b>	<b>3</b>
3.1	Read Resources . . . . .	3
3.2	Complete Tutorial 2 . . . . .	3
3.3	Complete Tutorial 3 . . . . .	3
<b>4</b>	<b>Part 2 — ALU</b>	<b>4</b>
4.1	1-Bit Logic Gates . . . . .	4
4.2	Muxes . . . . .	4
4.2.1	Multiplexer, commonly abbreviated as "mux" . . . . .	4
4.2.2	Decoder . . . . .	5
4.3	Adders . . . . .	5
4.3.1	1-Bit Adder . . . . .	5
4.3.2	8-Bit Adder . . . . .	5
4.4	8-Bit ALU . . . . .	5
<b>5</b>	<b>Part 3 — Advanced Combinational Logic</b>	<b>6</b>
5.1	Karnaugh Maps . . . . .	7
5.2	Boolean Logic Details . . . . .	7
5.3	Circuit Details . . . . .	7
<b>6</b>	<b>Autograder</b>	<b>7</b>
<b>7</b>	<b>Deliverables</b>	<b>7</b>
<b>8</b>	<b>Demos</b>	<b>8</b>
<b>9</b>	<b>Rules and Regulations</b>	<b>8</b>

9.1	General Rules . . . . .	8
9.2	Submission Conventions . . . . .	9
9.3	Submission Guidelines . . . . .	9
9.4	Syllabus Excerpt on Academic Misconduct . . . . .	9
9.5	Is collaboration allowed? . . . . .	10

# 1 Introduction

This project is designed to strengthen your knowledge of basic hardware elements and circuitry. The assignment is designed to build on each other, so work down the document linearly, otherwise you may not understand what is going on.

**Please read through the entire document before starting.** Often times things are elaborated on below where they are introduced, so reading the entire document can give you a better grasp on things. **Start early** and if you get stuck, there's always Piazza or come visit us in office hours.

## 2 Setup

The software you will be using for this project and all future circuit based assignments is called CircuitSim - an interactive circuit simulation package.

In order to use CircuitSim, you must have Docker up and running. If you do not have Docker, follow the instructions laid out in the installation guide found under Canvas  $\rightarrow$  Files  $\rightarrow$  Docker.

CircuitSim comes pre-installed on the Docker image, and should be accessible via the desktop. Please only use the CircuitSim through Docker to build your circuits as it is the correct version. **CircuitSim downloaded elsewhere may not be compatible with our grader. You have been warned.**

CircuitSim is a powerful simulation tool designed for educational use. This gives it the advantage of being a little more forgiving than some of the more commercial simulators. However, it still requires some time and effort to be able to use the program efficiently.

## 3 Part 1 — Introduction to CircuitSim

The first part of this project is designed to get you up to speed with CircuitSim. If you do not have CircuitSim running through Docker, see the setup section of this document to get there.

### 3.1 Read Resources

Read through the following resources

- CircuitSim Wires Documentation <https://ra4king.github.io/CircuitSim/docs/wires/>
- Tutorial 1: My First Circuit <https://ra4king.github.io/CircuitSim/tutorial/tut-1-beginner>

### 3.2 Complete Tutorial 2

Complete Tutorial 2 <https://ra4king.github.io/CircuitSim/tutorial/tut-2-xor>

Name the subcircuit `Tutorial 1`. Instead of saving your file `xor.sim` as mentioned in the tutorial, edit the existing file `tutorial1.sim`. Be sure you label your two inputs `a` and `b`, and your output as `c`.

### 3.3 Complete Tutorial 3

Complete Tutorial 3 <https://ra4king.github.io/CircuitSim/tutorial/tut-3-tunnels-splitters>

Name the subcircuit `Tutorial 2`, the input `in`, and the output `out`. Edit the file called `tutorial2.sim`.

## 4 Part 2 — ALU

Now that we have the basics down, we can move on to more complex circuits and logic. All computer processors have a very important component known as the Arithmetic Logic Unit (ALU). This component allows the computer to do, as the name suggests, arithmetic and logical operations. For this part, you're going to build an ALU of your own, along with creating some of the gates.

For this part of the project you will:

1. Create the standard logic gates (NAND, NOR, NOT, AND, OR)
2. Create an 8-input multiplexer and an 8-output decoder
3. Create a 1-bit full adder
4. Create an 8-bit full adder using your 1-bit full adder
5. Use your 8-bit full adder and other components to construct an 8-bit ALU

When building these circuits, restrictions have been placed on what you can use. These restrictions are listed at the beginning of each section. **Using anything not listed will result in heavy deductions.** You also need to have everything in its correctly named sub-circuit. More information on the sub-circuits is given below.

Use tunnels where necessary to make your designs more readable, but do not overdo it! For gates, multiplexers, decoders, and adders you can often make clean circuits by placing your components strategically rather than using tunnels everywhere.

### 4.1 1-Bit Logic Gates

#### Allowed Components: Wiring Tab and Circuits Tab

All of the circuits are found in the `gates.sim` file.

For this part, you will create a transistor-level implementation of the NAND, NOT, NOR, AND, and OR logic gates.

Remember for this section that you are only allowed to use the components listed in the Wiring section, along with any of the logic gates you are implementing in CircuitSim. For example, once you implement the NOT gate you are free to use that subcircuit in implementing other logic gates. Implementing the gates in the order of the subcircuit tabs can be the easiest option.

**Hint:** Start by creating the NAND and NOT gates from transistors. Then use this gate as a subcircuit for implementing the others.

**All of the logic gates must be within their named sub-circuits.**

### 4.2 Muxes

#### Allowed Components: Wiring Tab, Gates Tab, and Circuits Tab

All of the circuits are found in the `muxes.sim` file.

#### 4.2.1 Multiplexer, commonly abbreviated as "mux"

The multiplexer you will be creating has 8 1-bit inputs (labeled appropriately as A, B, C, ..., H), a single 3-bit selection input (SEL), and one 1-bit output (OUT). The multiplexer uses the SEL input to choose a specific input line for forwarding to the output. 000 should correspond to A, 001 should correspond to B, etc.

### 4.2.2 Decoder

The decoder you will be creating has a single 3-bit selection input (**SEL**), and eight 1-bit outputs (labeled **A**, **B**, **C**, ..., **H**). The decoder uses the **SEL** input to raise a specific output line. 000 should correspond to **A**, 001 should correspond to **B**, etc.

## 4.3 Adders

### Allowed Components: Wiring Tab, Gates Tab, and Circuits Tab

All of the circuits are found in the `alu.sim` file.

#### 4.3.1 1-Bit Adder

The full adder has three 1-bit inputs (**A**, **B**, and **CIN**), and two 1-bit outputs (**SUM** and **COUT**). The full adder adds  $A + B + CIN$  and places the sum in **SUM** and the carry-out in **COUT**.

For example:

$A = 0, B = 1, CIN = 0 \implies SUM = 1, COUT = 0$   
 $A = 1, B = 0, CIN = 1 \implies SUM = 0, COUT = 1$

**Hint:** Making a truth table of the inputs will help you.

#### 4.3.2 8-Bit Adder

You should daisy-chain 8 of your 1-bit full adders together in order to make an 8-bit full adder.

This circuit should have two 8-bit inputs (**A** and **B**) for the numbers you're adding, and one 1-bit input for **CIN**. The reason for the **CIN** has to do with using the adder for purposes other than adding the two inputs.

There should be one 8-bit output for **SUM** and one 1-bit output for **COUT**.

## 4.4 8-Bit ALU

### Allowed Components: Wiring Tab, Gates Tab, Plexer Tab, and Circuits Tab

You will create an 8-bit ALU with the following operations. Feel free to use the circuits you made in previous parts of this lab to implement the following operations.

000 add	$[A + B]$
001 sub	$[A - B]$
010 min	$[\min(A, B)]$
011 barrelShifter	See below
100 floorPowerOf2	See below
101 isMultipleOf8	$[A \% 8 == 0]$
110 multiplyBy3	$[A * 3]$
111 isOdd	$[A \% 2 == 1]$

**barrelShifter:** For this operation, you will need to implement a barrel shifter. At its core, a barrel shifter is a circuit that allows you to shift the bits of a word by a certain amount using only combinational logic. For the barrel shifter in this project, you will need to create an 8-bit barrel shifter that will shift the bits of A to the left by the amount specified in the SHIFT input pin in the alu.sim file.

Examples:

```
A = 00101111, SHIFT = 010 => return 10111100
A = 11110000, SHIFT = 001 => return 11100000
```

Hint: Think about how you can use multiplexers to implement this shifting! You may need quite a few of them.

**floorPowerOf2:** To elaborate, this operation should return the 8-bit representation of the value that is produced when C is floored to the nearest power of 2. If there is no valid result to return (no power of 2 is produced when C is floored) return 0. Keep in mind that C is given in a 4-bit representation.

Examples:

```
C = 0110 => return 00000100
C = 1100 => return 00000000
```

Notice that **barrelShifter**, **floorPowerOf2**, **isMultipleOf8**, **multiplyBy3**, and **isOdd** only operate on the A or C input. They should **NOT** rely on B being a particular value.

This ALU has two 8-bit inputs for A and B, one 4-bit input for C, one 3-bit input for SHIFT, and one 3-bit input for OP, which is the op-code for the operation in the list above. It has one 8-bit output named OUT.

The provided autograder will check the op-codes according to the order listed above (add (000), sub (001), etc.) and thus it is important that the operations are in this exact order.

No partial credit will be given for incorrect outputs for logic gates, plexers, or adders. However, for the ALU, partial credit will be awarded on a per-operation basis, wherein each operation must perform successfully to be awarded credit. Because of this, we urge you to check your score before the due date.

## 5 Part 3 — Advanced Combinational Logic

In a not-so-imaginary world, each circuit in a house can only output so much power before blowing a fuse. However, you could also accomplish something similar with a smarthome-style set up and the Internet of Things, and cutting the power if too many things are in use for the circuit to be safe. We are going to do neither of those things and instead solve it with a bit of good ole combinational logic! For the average 15A, 120V circuit in a residential setting, there is a theoretical max output of 1800W before bad things happen. The devices on the circuit that can be turned on or off are shown in the table below:

<i>Fridge **</i>	1000W, 400W
<i>Microwave</i>	600W
<i>Lights</i>	180W
<i>Toaster</i>	800W
<i>CoffeeMaker</i>	600W

For the fridge, we never want to leave our fridge off if we have the chance, so instead of thinking of it being on or off, **we will think of it as the F signal high/1 representing the fridge running, only consuming 400W, and the F signal low/0 representing the fridge being started up, consuming 1000W.** For this reason we will use 2 separate K-maps, one for when the fridge is already running, and one for when we also need to consider it starting up. After that we can use some combinational logic to turn this into a control circuit! The output of the K-map and your control circuit should be if power can be delivered to

all devices considering what the fridge is doing, with high/1 being yes the power can be supplied and low/0 being that the circuit would be dangerous and power should not be supplied.

**As always, do not change/delete any of the input/output pins.**

## 5.1 Karnaugh Maps

While it is not a deliverable, making 2 K-maps and reducing boolean expressions will make this circuit significantly easier to design. To aid this, we have provided a template for both K-maps below:

$F$	$M'L'$	$M'L$	$ML$	$ML'$
$T'C'$				
$T'C$				
$TC$				
$TC'$				

$F'$	$M'L'$	$M'L$	$ML$	$ML'$
$T'C'$				
$T'C$				
$TC$				
$TC'$				

## 5.2 Boolean Logic Details

For this part of the project, we are asking that you approach this problem in **sum of products format**. This means that after your reductions using the K-maps, you should have something in the format

$$D = A'B + C$$

**before** attempting to build the circuit. Failure to do so can lead to complications in your circuit that prevent the reduction we are looking for.

## 5.3 Circuit Details

To prevent trivialization of this assignment, we have placed a few restrictions:

- All of this circuit should be contained in the **kitchen.sim** file
- You can **only** use NOT, AND, and OR gates (in addition to wiring, text labels and the like)
- You should try to reduce the amount of AND and OR gates as much as possible.

Hint: The K-maps do this for you!

## 6 Autograder

To run the autograder, run

```
java -jar project1-tester-1.0.jar
```

at a command prompt in the same directory as all your **.sim** files. This is the same autograder that Gradescope uses, but is much easier and faster to use.

## 7 Deliverables

Please submit the follow files:

1. tutorial1.sim	
2. tutorial2.sim	umbrella
3. gates.sim	NOT, NAND, NOR, AND, OR
4. muxes.sim	Decoder, MUX
5. alu.sim	1-Bit Adder, 8-Bit Adder, 8-Bit ALU
6. kitchen.sim	Advanced Combinational Logic

to Gradescope under the assignment “Project 1”.

**Note:** The autograder may not reflect your final grade on this assignment. We reserve the right to update the autograder as we see fit when grading.

## 8 Demos

**This project will be demoed.** Demos are designed to make sure that you understand the content of the project and related topics. They may include technical and/or conceptual questions.

- Sign up for a demo time slot via Canvas **before** the beginning of the first demo slot. This is the only way you can ensure you will have a slot.
- If you cannot attend any of the predetermined demo time slots, e-mail the Head TA **before** the beginning of the first demo slot.
- If you know you are going to miss your demo, you can cancel your slot on Canvas with no penalty. However, you are **not** guaranteed another time slot. You cannot cancel your demo within 24 hours or else it will be counted as a missed demo.
- Your overall project score will be  $((\text{project\_score} * 0.5) + (\text{demo\_score} * 0.5))$ , meaning if you received a 90% on your project, but a 30% on the demo you would receive an overall score of 60%. **If you miss your demo you will not receive any of these points and the maximum you can receive on the project is 50%.**
- You will be able to makeup one of your demos at the end of the semester for half credit.

## 9 Rules and Regulations

### 9.1 General Rules

1. Although you may ask TAs for clarification, you are ultimately responsible for what you submit. This means that (in the case of demos) you should come prepared to explain to the TA how any piece of code you submitted works, even if you copied it from the book or read about it on the internet.
2. Please read the assignment in its entirety before asking questions.
3. Please start assignments early, and ask for help early. Do not email us a few hours before the assignment is due with questions.
4. If you find any problems with the assignment, it would be greatly appreciated if you reported them to the author (which can be found at the top of the assignment). Announcements will be posted if the assignment changes.



## 9.2 Submission Conventions

1. When preparing your submission you may either submit the files individually to Canvas/Gradescope or you may submit an archive (zip or tar.gz only please) of the files. Both ways (uploading raw files or an archive) are exactly equivalent, so choose whichever is most convenient for you.
2. Do not submit links to files. The autograder does not understand it, and we will not manually grade assignments submitted this way as it is easy to change the files after the submission period ends.

## 9.3 Submission Guidelines

1. You are responsible for turning in assignments on time. This includes allowing for unforeseen circumstances. If you have an emergency let us know **IN ADVANCE** of the due time supplying documentation (i.e. note from the dean, doctor's note, etc). Extensions will only be granted to those who contact us in advance of the deadline and no extensions will be made after the due date.
2. You are also responsible for ensuring that what you turned in is what you meant to turn in. After submitting you should be sure to download your submission into a brand new folder and test if it works. No excuses if you submit the wrong files, what you turn in is what we grade. In addition, your assignment must be turned in via Canvas/Gradescope. Under no circumstances whatsoever we will accept any email submission of an assignment. Note: if you were granted an extension you will still turn in the assignment over Canvas/Gradescope.
3. You are additionally responsible for ensuring that the collaborators list you have provided in your submission is accurate.
4. Projects turned in late receive partial credit within the first 48 hours. We will take off 30% of the points for a project submitted between 0 and 24 hours late, and we will take off 50% of the points for a project submitted between 24 and 48 hours late. We will not accept projects turned in over 48 hours late. This late policy is also in the syllabus.
5. You alone are responsible for submitting your project before the assignment is due; neither Canvas/Gradescope, nor your flaky internet are to blame if you are unable to submit because you banked on your computer working up until the deadline.

## 9.4 Syllabus Excerpt on Academic Misconduct

Academic misconduct is taken very seriously in this class.

1. Students are expected to have read and agreed to the Georgia Tech Honor Code, see <http://osi.gatech.edu/content/honor-code>.
2. Suspected plagiarism will be reported to the Division of Student Life office. It will be prosecuted to the full extent of Institute policies.
3. A student must submit an assignment or project as his/her own work (this is what is expected of the students).
4. Using code from GitHub, via Googling, from Stack Overflow, etc., is plagiarism and is not permitted. Do not publish your assignments on public repositories (i.e., accessible to other students). This is also a punishable offense.
5. Although discussion among the students through piazza and other means are encouraged, the sharing of work is plagiarism. If you are not sure about it, please ask a TA or stop by the instructor's office during the office hours.

6. You must list any student with whom you have collaborated in your submission. Failure to list collaborators is a punishable offense.
7. TAs and Instructor determine whether the project is plagiarized. Trust us, it is really easy to determine this....

## 9.5 Is collaboration allowed?

Collaboration is allowed on a high level, meaning that you may discuss design points and concepts relevant to the homework with your peers, share algorithms and pseudo-code, as well as help each other debug code. What you should not be doing, however, is pair programming where you collaborate with each other on a single instance of the code. Furthermore, sending an electronic copy of your homework to another student for them to look at and figure out what is wrong with their code is not an acceptable way to help them, because it is frequently the case that the recipient will simply modify the code and submit it as their own. Consider instead using a screen-sharing collaboration app, such as Bluejeans, to help someone with debugging if you're not in the same room.

Any of your peers with whom you collaborate in the above fashion must be properly added to your **collaborators.txt** file. Collaborating with another student without listing that student as a collaborator is considered plagiarism.

